

shunt feedback
Op-amp feedback

Op-amp feedback
Op-amp feedback

approximate
gain of

effect is called

due to A₁

efficiency proportional

decreased

$R_L = R_{L1} R_{L2}$




difference of A₂

by containing

selected in

parameters.

-h_{FE} (parallel)
R_{in}

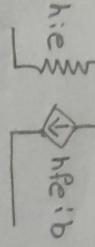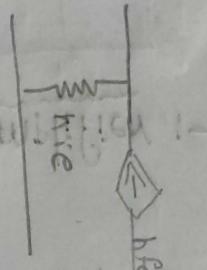
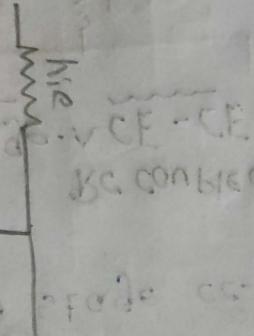
S.No	Configuration	H-parameter equivalent	Parameters
1.	CE configuration		$R_i = h_{ie}$ $A_T = -h_{FE}$ $A_V = \frac{A_T \times R_L}{R_i}$ $R_o = \infty$
2.	CB configuration		$R_i = h_{ie}$ $A_T = \frac{h_{fe}}{1+h_{fe}}$ $A_V = \frac{A_T \times R_L}{R_i}$ $R_o = \infty$
3.	CC configuration.		$R_i = h_{ie} + (1+h_{fe})R_L$ $A_T = 1+h_{fe}$ $A_V = \frac{A_T \times R_L}{R_i}$; $R_o = \frac{R_S + h_{ie}}{1+h_{fe}}$

* Loading Effect :-
Let us consider a two amplifier connected in cascade.

UNIT-2

5 MARKS

Probable Topics :- Vec Sums etc.

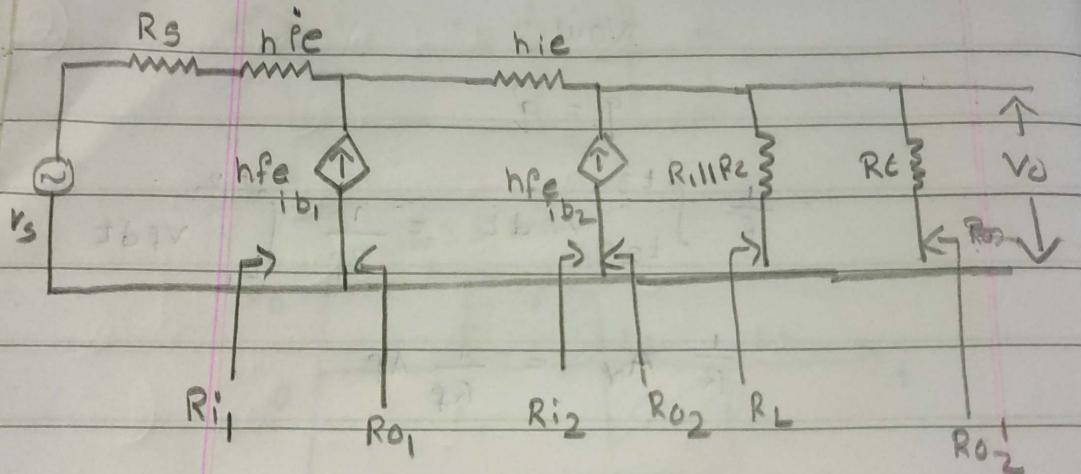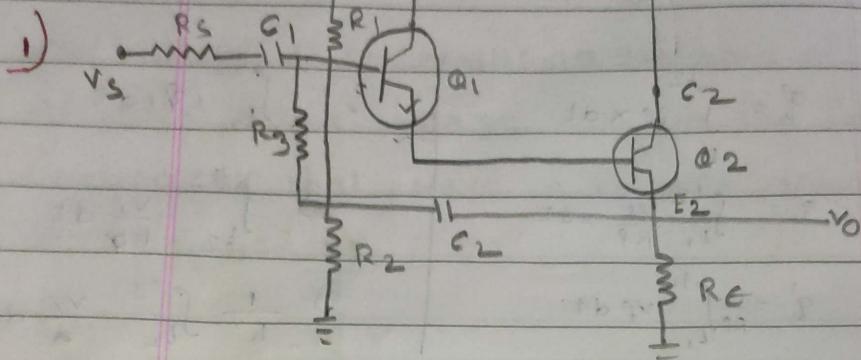

Here Stage 1 is CC Amplifier

Stage 2 is CC Amplifier

Note:- Before doing analysis pls verify the
CC Amplifier table values.

Stage-2 :-

$$A_{I2} =$$

$$R_{I2} =$$

$$A_{V2}$$

$$R_{O2}$$

$$S$$

Stage-2 :-

$$AI_2 = 1+hfe$$

$$\begin{aligned} RI_2 &= hie + (1+hfe) RL \\ &= (1+hfe) RL \quad (\because hie \ll (1+hfe)) \end{aligned}$$

$$AV_2 = \frac{AI_2 \times RL}{RI_2}$$

$$\Rightarrow \frac{(1+hfe) RL}{(1+hfe) RL} = 1.$$

$$Ro_2 \Rightarrow \frac{RS + hie}{1+hfe} \Rightarrow \frac{hie}{1+hfe}$$

$$Ro_2' \Rightarrow Ro_2 || RL \cong Ro_2$$

Stage-1 :-

$$AI_1 = 1+hfe$$

$$RI_1 = hie + (1+hfe) RL$$

$$\Rightarrow (1+hfe) RL.$$

$$AV_1 \Rightarrow \frac{AI_1 \times RL}{RI_1} \Rightarrow \frac{(1+hfe) \times RL}{(1+hfe) RL} = 1$$

$$Ro_1 \Rightarrow \frac{RS + hie}{1+hfe} \Rightarrow \frac{hie}{1+hfe}$$

$(\because RS \ll hie)$

Loading Effect :-
Let us consider a two amplifier connected in cascade.

Overall Analysis :-

$$AI = (1+hfe)(1+hfe) = (1+hfe)^2$$

$$RI = [(1+hfe) RL] [(1+hfe) R2]$$

$$\Rightarrow (1+hfe)^2 RL^2$$

$$AV = 1 \times 1 = 1$$

$$Ro = \frac{hie}{1+hfe} \times \frac{hie}{1+hfe}$$

2)


There are three types of coupling:-

i) RC coupling

ii) Transformer coupling


iii) Direct coupling.

i) RC coupling :-

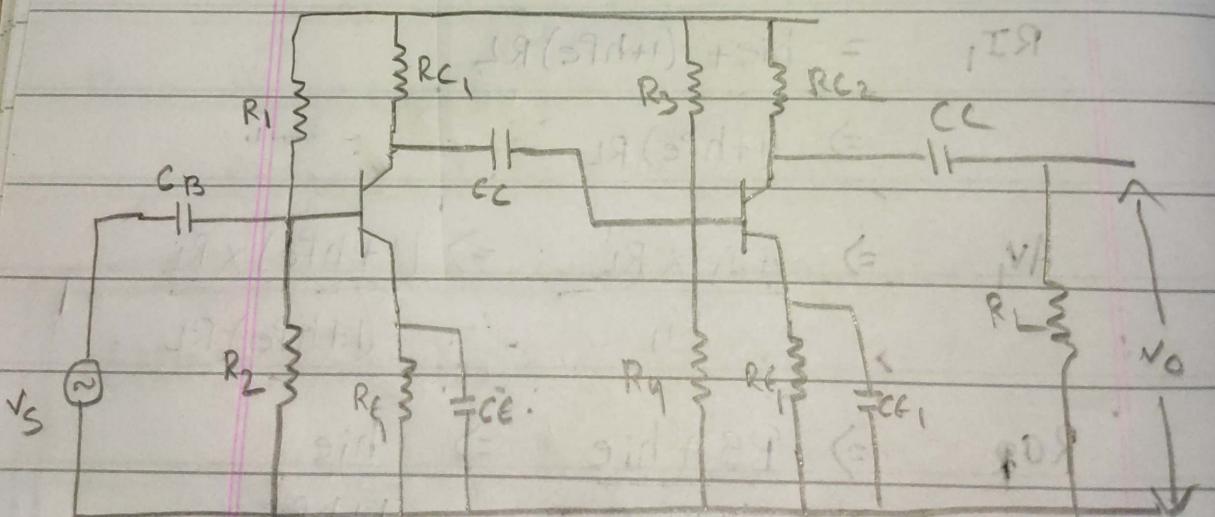


- i) This is Q-point factor
- ii) Due to wide range
- iii) The ft

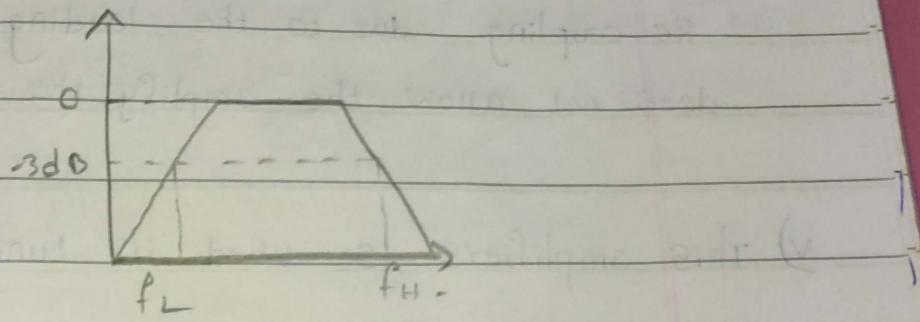- i) This RC coupling does not effect the Q-point of stage 2 because the coupling factor is blocks the first stage voltage
- ii) Due to this blocking it will produce wide band frequency response. So they are used in complete ^{audio} amplifier frequency bands
- iii) This total response will drops at low frequency because the coupling capacitor will drops the high frequency.



ii) Transformer coupling

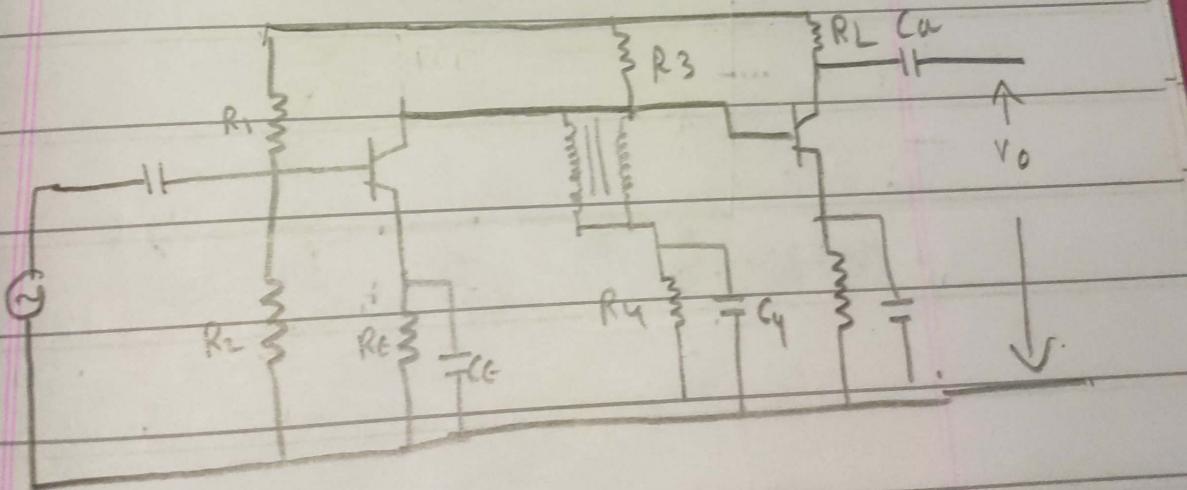


- i) The output of first stage is coupled with the input of second stage through transformer is


* Loading Effect :-
Let us consider two amplifiers connected in cascade.

called transformer amplifier

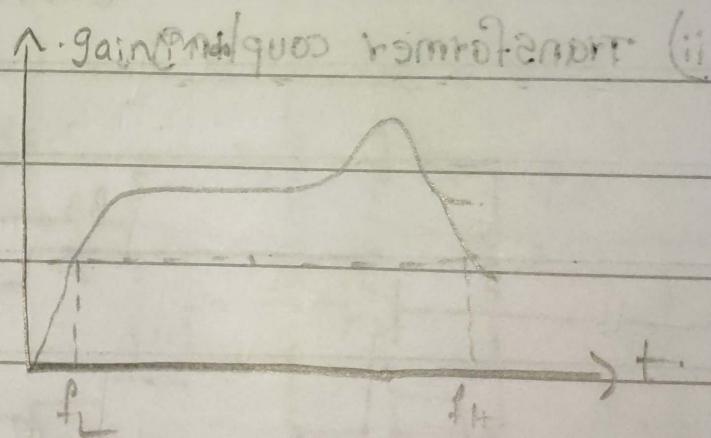
- i) This type of coupling is used to match the impedance between the output of first stage and input of second stage.
- ii) Direct
- iii) This transformer coupling does not effect the Q-point of next stage amplifier.
- iv) The frequency response of transformer coupling amplifier is low when compared to the RC coupling due to the loading inductance does not allow the amplify the signal.
- v) This amplifiers is used in tuned amplifiers



iii) Direct coupling:-

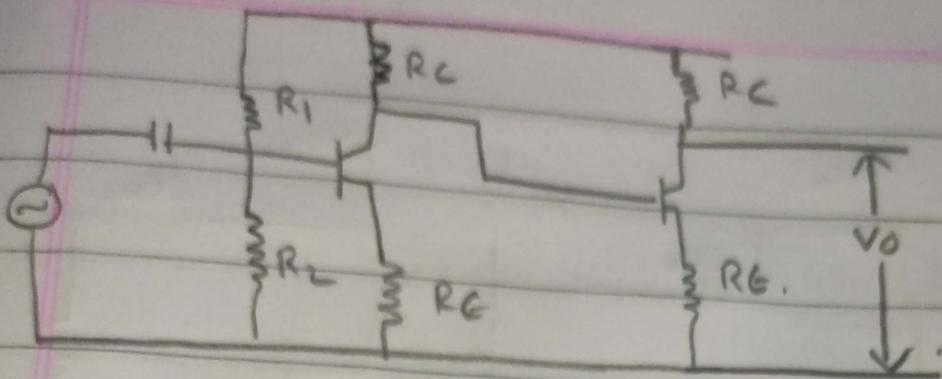

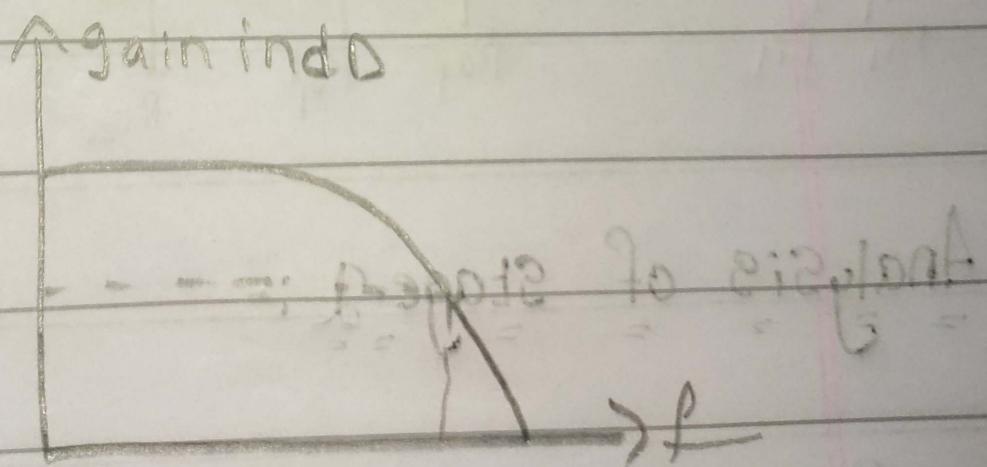- i) The output of first stage is directly coupled with the input of second stage.
- ii) The direct coupling allows the dc collectors of first stage and pass through base of second stage. It will effect the biasing condition.



3 QUESTION


* Boot strap Emitter Follower:-

Generally in the Darlington pair amplifier the resistance $R_i = R_{i1} = (1+hfe)(R_0 \parallel R_{12})$

If we consider the biasing resistance then the resistance decreases because biasing resistance values less i.e.

$$(R_0 \parallel R_{12}) \ll R_i$$

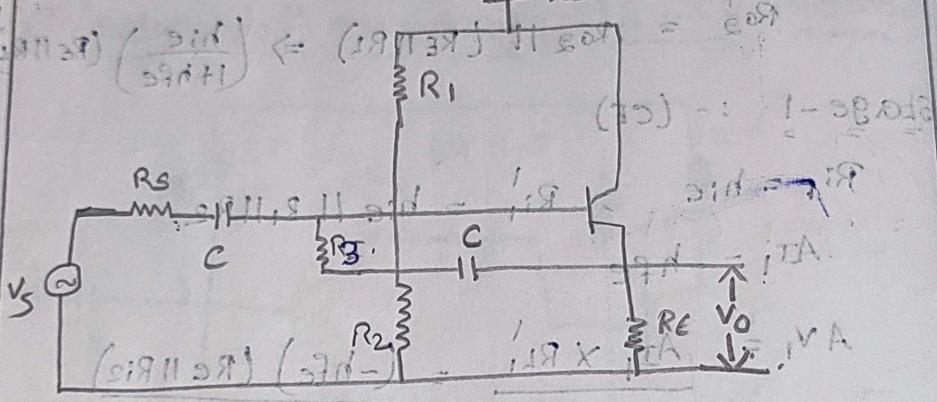In order to avoid that problem a technique is called Boot strap Emitter Follower circuit



A circuit which include two components (A_3, c) to the CC Amplifier is known as Emitter follower circuit. The resistor R_3 is connected b/w base of transistor and combination of $R_1 \& R_2$ and capacitor C is connected b/w emts of the transistor.

For DC signal capacitor doesn't allows and binary is provided of R_1, R_2, R_3 .


For AC Signals the bottom of R_3 is connected to the top of R_3 is connected to IP.

Miller's theorem states that the Impedance is connected b/w two nodes then it is represented by two components one is connected to input w.r.t ground another one is connected with output with respect to ground.

$$\frac{Z}{1-AV} ; \quad \frac{Z}{1-\frac{1}{AV}}$$

i.e. $\frac{R_3}{1-AV} ; \quad \frac{R_3}{1-\frac{1}{AV}}$

AC Equivalent circuit :-

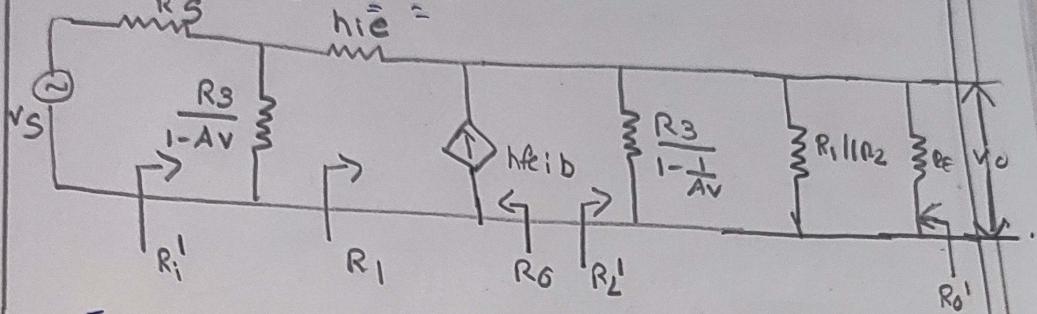

For CC Amplifier the voltage gain is 1 which means circuit i.e

$$\frac{R_3}{1-AV} ; \quad \frac{R_3}{1-\frac{1}{AV}} \rightarrow \infty [o.c.]$$

$$R_i = h_{ie} + (1+h_{fe}) R_L'$$

$$R_i = (1+h_{fe}) R_L'$$

$$R_i = (1+h_{fe}) (R_1 || R_2 || R_E)$$

$$R_o = \frac{h_{ie} + R_S}{(1+h_{fe})}$$



$$R_o' \Rightarrow R_o / |R_L'| \Rightarrow R_o' \Rightarrow \frac{h_{ie} + R_S}{1+h_{fe}} || (R_1 || R_2 || R_E)$$

$$A_I \Rightarrow 1+h_{fe}$$

$$A_V \Rightarrow \frac{A_I \times R_L'}{R_i} = \frac{(1+h_{fe})(R_1 || R_2 || R_E)}{(1+h_{fe})(R_1 || R_2 || R_E) + 1} \approx 1$$

4) Same as the 1st question.

5) TWO stage RC coupled Amplifier:-

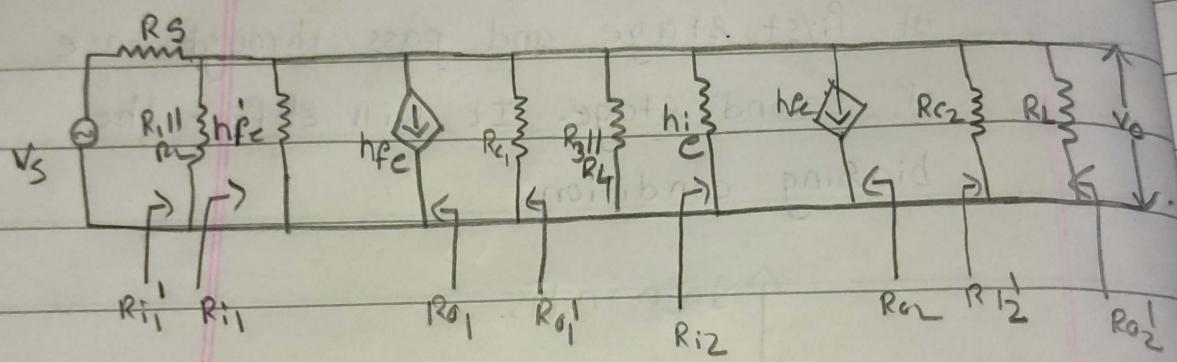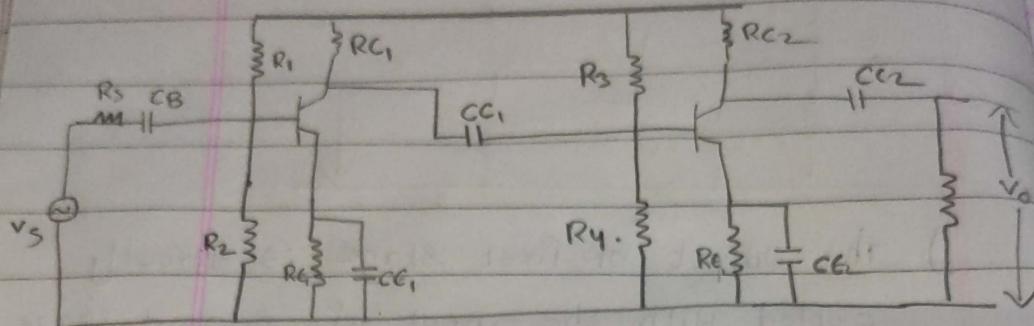

Analysis of Stage-2 :-

$$R_{i2} = h_{ie}$$

$$A_{I2} = -h_{fe}$$

$$A_{V2} = \frac{A_{I2} \times R_L}{R_{i2}} \Rightarrow \frac{-h_{fe} \times (R_{C2} + R_L)}{h_{ie}}$$

$$R_{o2} = \infty$$

$$R_{o2}' = \infty || R_{C2} || R_L \Rightarrow R_{C2} || R_L$$

Analysis of stage-1 :-

$$R_{i1} = h_{ie}$$

$$A_{I1} = -h_{fe}$$

$$R_{o1}' = R_1 \parallel R_2 \parallel h_{fe}.$$

$$AV_1 = \frac{A_{I1} \times R_{L1}'}{R_{o1}'} \Rightarrow \frac{-h_{fe} (R_{C1} \parallel R_{31} \parallel R_{41} \parallel h_{ie})}{h_{ie}}$$

$$R_{G1} = \infty$$

$$R_{o1}' = \infty \parallel R_{C1} = R_{Cf}.$$

Overall Analysis :-

$$R_i = R_{i1} = R_1 \parallel R_2 \parallel h_{ie}.$$

$$R_o = R_{o2}' = R_{C2} \parallel R_L$$

$$AV = AV_1 \times AV_2$$


$$\Rightarrow \left[\frac{-h_{fe} (R_{C1} \parallel R_{31} \parallel R_{41} \parallel h_{ie})}{h_{ie}} \right] \left[\frac{-h_{fe} (R_{C2} \parallel R_L)}{h_{ie}} \right]$$

$$A_I \Rightarrow -h_{fe} \times -h_{fe} = (h_{fe})^2$$


6th QUESTION

* Two Stage CE-CB Amplifier (cascaded)

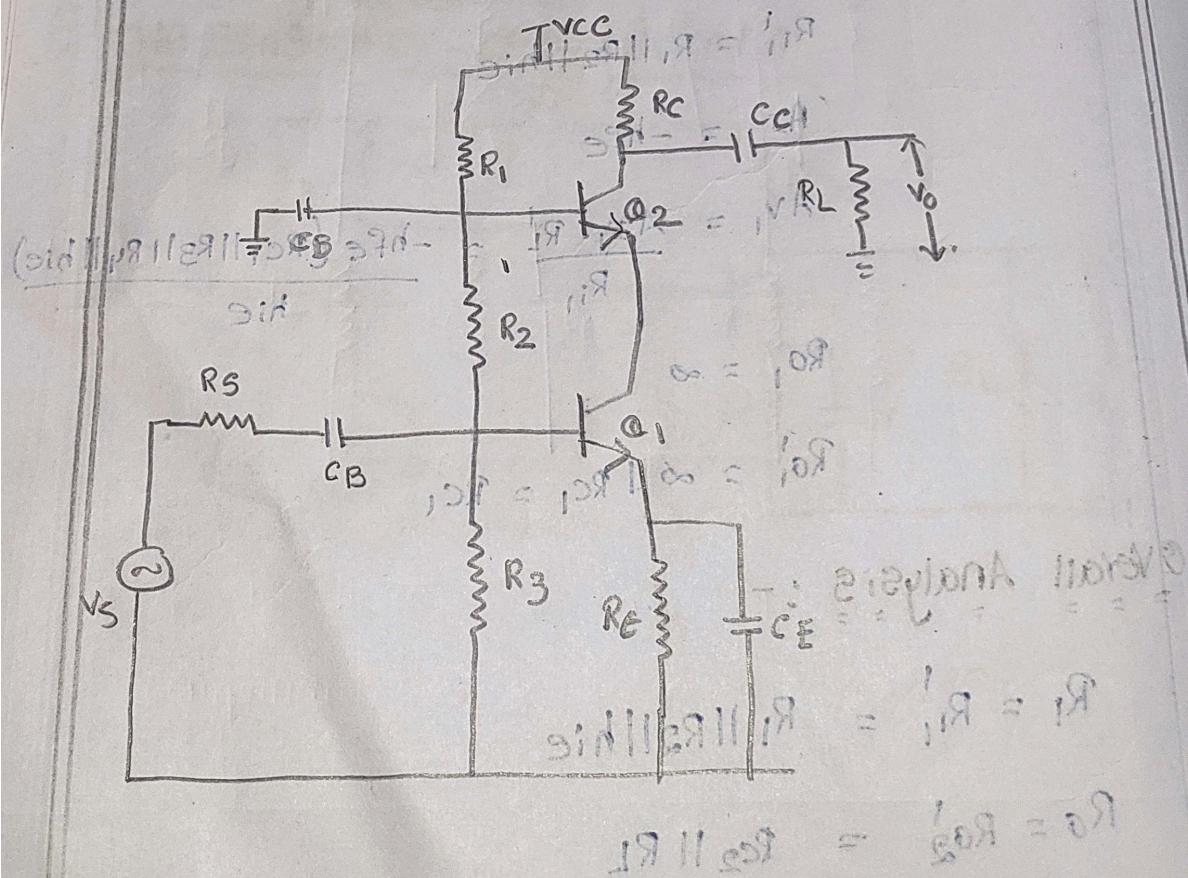- The cascading of CE-CB amplifier is also known as cascaded amplifier.
- which consists of CE amplifier series with CB amplifier.



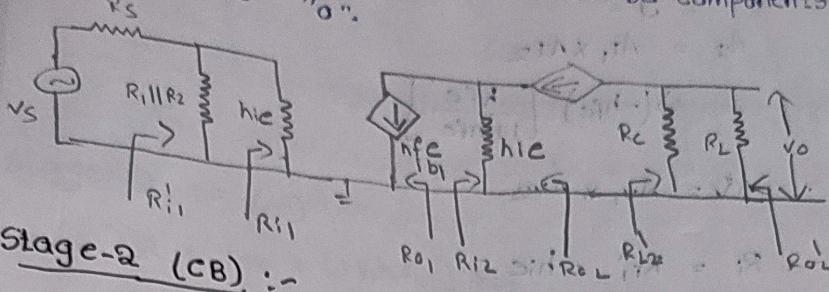To draw the AC equivalent circuit DC components are said to "o".



Stage-2 (CB) :-

$$R_{i2} = \frac{h_{ie}}{1+h_{fe}}$$

$$A_{I2} = \frac{h_{fe}}{1+h_{fe}}$$

$$AV_2 = \frac{A_{I2} \times R_L'}{R_{i2}} = \left(\frac{h_{fe}}{1+h_{fe}} \right) (R_C || R_L)$$

$$R_{O2}' = \infty || R_C || R_L \Rightarrow R_C || R_L.$$

$$R_{O2} = \infty$$

$$R_{O2}' = \infty || R_C || R_L \Rightarrow R_C || R_L.$$

Stage-1 (CE) :-

$$R_{i1} = h_{ie}$$

$$R_{i1}' = h_{ie} || R_2 || R_3$$

$$A_{I1} = -h_{fe}$$

$$AV_1 = \frac{A_I \times R_L'}{R_{i1}} = \frac{(-h_{fe})(R_{i2})}{R_{i1}} \Rightarrow$$

DC biasing involves $(-h_{fe}) \left(\frac{h_{ie}}{1+h_{fe}} \right)$
AC analysis involves h_{ie} .

$$R_{O1} = \infty$$



Overall Analysis

$$A_I = A_{I_1} \times A_{I_2}$$

$$\Rightarrow (-h_{fe}) \left[\frac{h_{fe}}{1+h_{fe}} \right]$$

$$A_V = A_{V_1} \times A_{V_2}$$

$$R_i = R_{ii}' = h_{ie}$$


$$R_o = R_{o2}' = R_c || R_L$$

$$A_{VG} = \frac{A_V \cdot R_i'}{R_s + R_{ii}'}$$


$$A_{IS} = \frac{A_I R_S}{R_s + R_{ii}'}$$


7 QUESTION

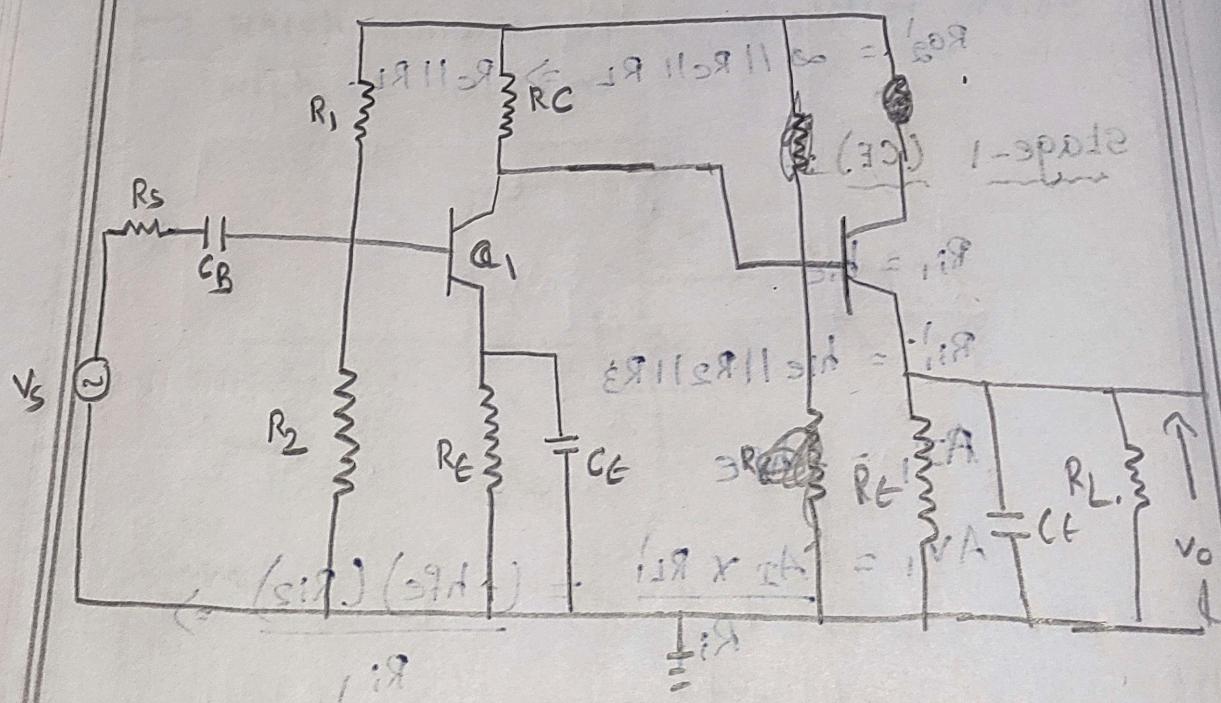* AC Analysis of Two stage CE - CC Amplifier



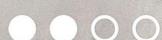→ To draw AC equivalent circuit DC Components are set to be zero.



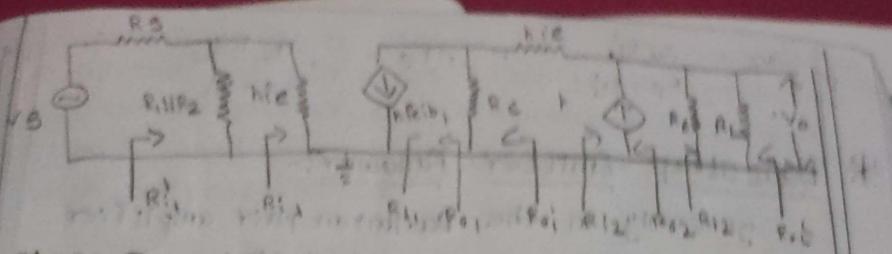

Stage - 2 :- (ce)

$$R_{o2} = h_{ie} + (1+h_{fe}) R_L \quad \text{but we have } R_L \\ \Rightarrow h_{ie} + (1+h_{fe}) (R_E || R_L)$$

$$A_{I2} = 1+h_{fe}$$

$$AV_2 = \frac{A_{I2} \times R_{L2}}{R_{o2}} \Rightarrow \frac{(1+h_{fe})(R_E || R_L)}{h_{ie} + (1+h_{fe})(R_E || R_L)}$$

$$R_{o2} = \frac{h_{ie}}{1+h_{fe}}$$

$$R_{o2}' = R_{o2} || (R_E || R_L) \Rightarrow \left(\frac{h_{ie}}{1+h_{fe}} \right) (R_E || R_L)$$

Stage - 1 :- (CE)

$$R_{i1} = h_{ie} ; R_{i1}' = h_{ie} || R_1 || R_2$$

$$A_{I1} = -h_{fe}$$

$$AV_1 = \frac{A_{I1} \times R_{L1}'}{R_{i1}} = \frac{(-h_{fe})(R_E || R_{i2}')}{h_{ie}}$$

$$R_{o1} = \infty \quad \text{as there is no load for stage 1}$$

$$\therefore R_{o1}' = \infty || R_C = R_C \quad \text{as CA voltage is zero}$$

Overall Analysis :-

$$R_i = R_{i1}' = h_{ie} || R_1 || R_2$$

$$R_o = R_{o2}' = \left(\frac{h_{ie}}{1+h_{fe}} \right) (R_E || R_C)$$

$$AV = AV_1 \times AV_2$$

$$\therefore A_I = A_{I1} \times A_{I2} \Rightarrow (-h_{fe})(1+h_{fe})$$

8) Given that

$$h_{FE} = 100 \quad R_S = 1\text{ k}\Omega$$

$$h_{ie} = 2\text{ k}\Omega \quad R_E = 25\text{ k}\Omega$$

$$h_{re} = h_{oe} = 0 \quad R_C = 100\text{ }\Omega$$

Given that it is the cascode circuit
i.e. CE - CB

$$A_I = [-h_{FE}] \left[\frac{h_{FE}}{1+h_{FE}} \right]$$

$$-100 \times \frac{100}{101} \Rightarrow -100 \times 0.99 \\ \Rightarrow -99.$$

$$AV = AV_1 \times AV_2$$

$$\Rightarrow \left[\frac{(-h_{FE}) \left(\frac{h_{ie}}{1+h_{FE}} \right)}{h_{ie}} \right] \times \left[\frac{\frac{h_{FE}}{1+h_{FE}} (R_C || R_L)}{\frac{h_{FE}}{1+h_{FE}}} \right]$$

$$\Rightarrow \left[\frac{(-100) \left(\frac{2 \times 10^3}{101} \right)}{2 \times 10^3} \right] \left[\frac{100 \times 1000}{100 + 1000} \right]$$

$$\Rightarrow \left[\frac{-0.99 \times 2 \times 10^3}{2 \times 10^3} \right] \left[\frac{100000}{1100} \right]$$

$[-0.99] [90.90]$

-90.

$$A_{vS} \Rightarrow \frac{A_v \times R_i'}{R_S + R_i'} \quad \left[\begin{array}{l} \text{From Analysis} \\ R_i' = h_{ie} \end{array} \right]$$

$$\Rightarrow \frac{A_v \times h_{ie}}{R_S + h_{ie}}$$

$$\Rightarrow \frac{-90 \times 2 \times 10^3}{1 \times 10^3 + 2 \times 10^3}$$

$$\Rightarrow \frac{-180 \times 10^3}{3000 + 2000} \Rightarrow \frac{-180 \times 10^3}{3000} \Rightarrow \frac{-180 \times 10^3}{3 \times 10^3}$$

$$\Rightarrow -60.$$

$$R_i \Rightarrow h_{ie} \Rightarrow 2k\Omega$$

$$\Rightarrow 2 \times 10^3$$

$$R_O \Rightarrow R_{O2}' \Rightarrow R_C || R_L$$

$$\Rightarrow \frac{100 \times 1000}{100 + 1000} \Rightarrow 90.90 \quad \approx$$